

Name _____

Date _____

Part 1; Q1-6 _____ of 102

Part 2; Q 7-10 _____ of 87

Digital Electronics Exam 1

1. Convert the following to binary. (2 points each)

19 _____ 12 _____ 6 _____ 16 _____

2. Convert the following to decimal. (2 points each)

11011 _____ 1101 _____ 11000 _____ 11010 _____

3. Complete each of the items in the table. (5 points each)

	AND	OR	NOT																																						
Switch Based Circuit																																									
Boolean Expression																																									
Truth Table	<table><tr><th colspan="2">INPUTS</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>L</th></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr></table>	INPUTS		OUTPUT	A	B	L										<table><tr><th colspan="2">INPUTS</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>L</th></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td></tr></table>	INPUTS		OUTPUT	A	B	L										<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>L</th></tr><tr><td></td><td></td></tr><tr><td></td><td></td></tr></table>	INPUT	OUTPUT	A	L				
INPUTS		OUTPUT																																							
A	B	L																																							
INPUTS		OUTPUT																																							
A	B	L																																							
INPUT	OUTPUT																																								
A	L																																								
Symbol																																									

4. Alongside each acronym, place the words that each stands for. (2 points each)

NC _____

CMOS _____

TTL _____


IC _____

LSB _____

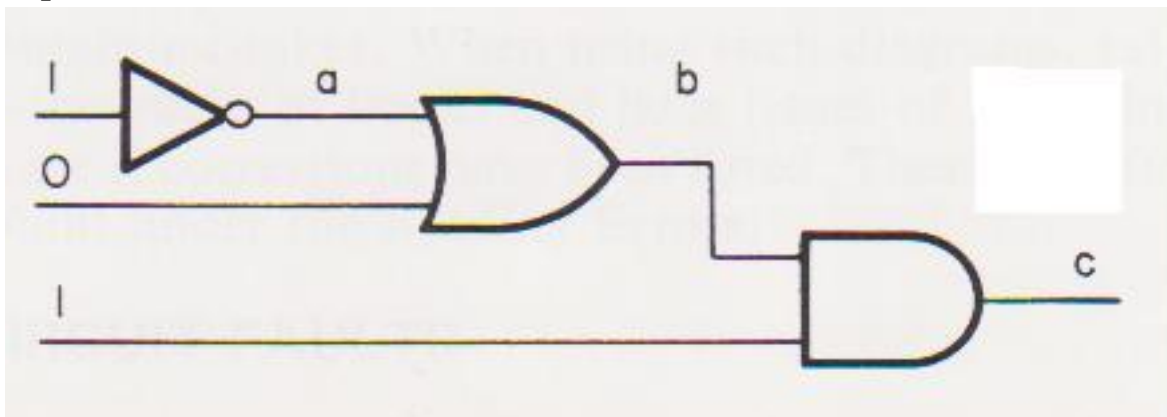5. Number the binary digits on the set of lines immediately beneath each of the binary digits.
On the line beneath that, indicate the place value of that digit.
(5 points each part, 10 points total)

1 0 1 1 0 0 1 1 0 1

- 6 Record the output that will occur at points a, b and c given the inputs shown.
(2 points each)




a = _____

b = _____


c = _____

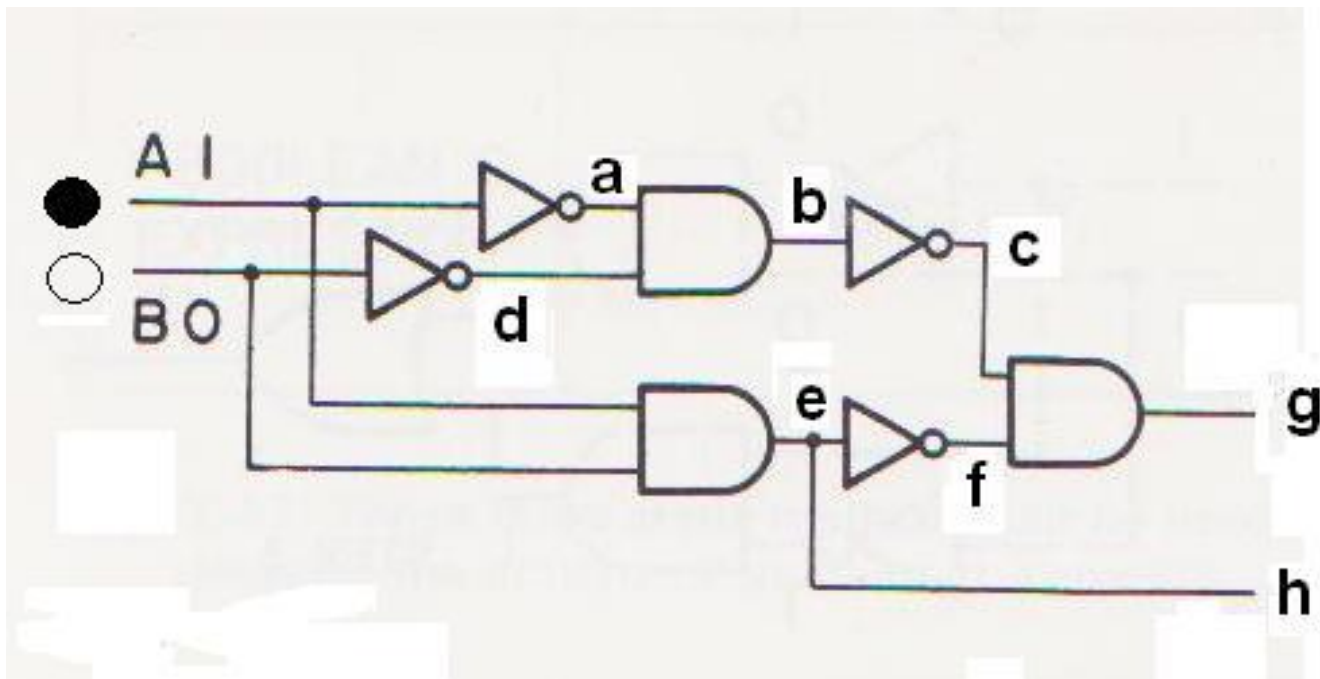7. Fill in the value that will be present at each of the points indicated. (5 points each)




a. _____	d. _____	g. _____
b. _____	e. _____	h. _____
c. _____	f. _____	

8. (10 points each)

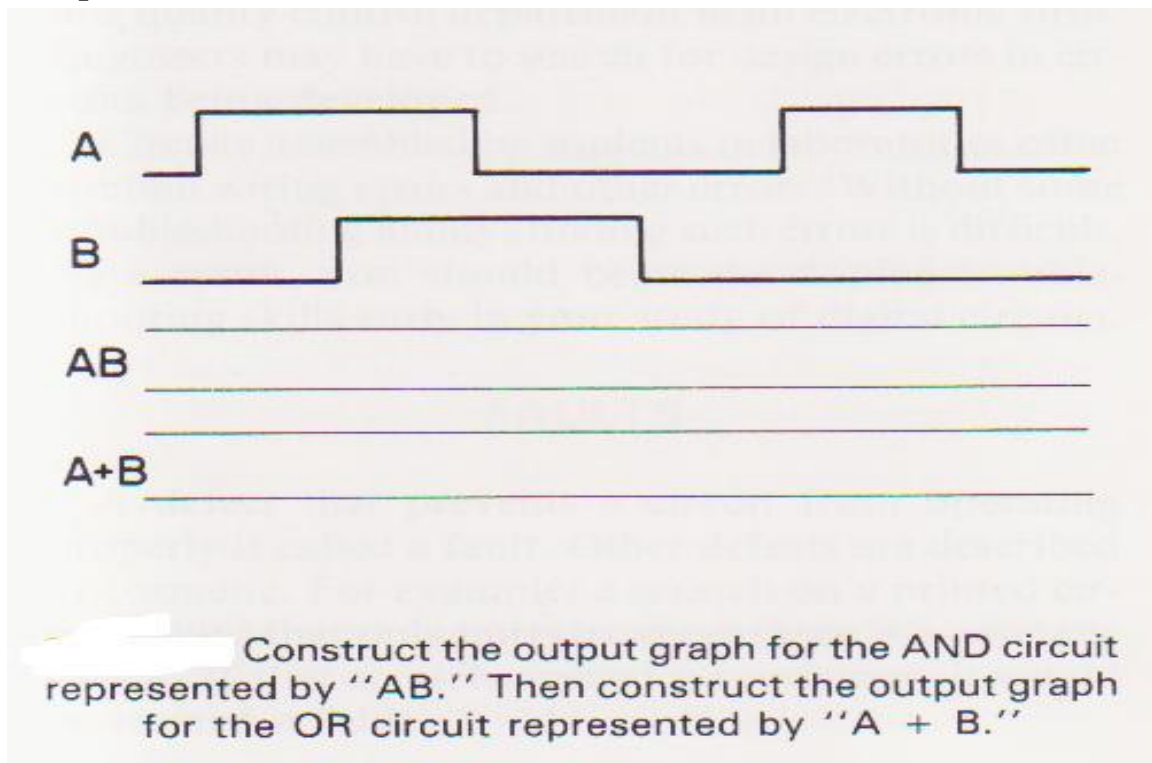

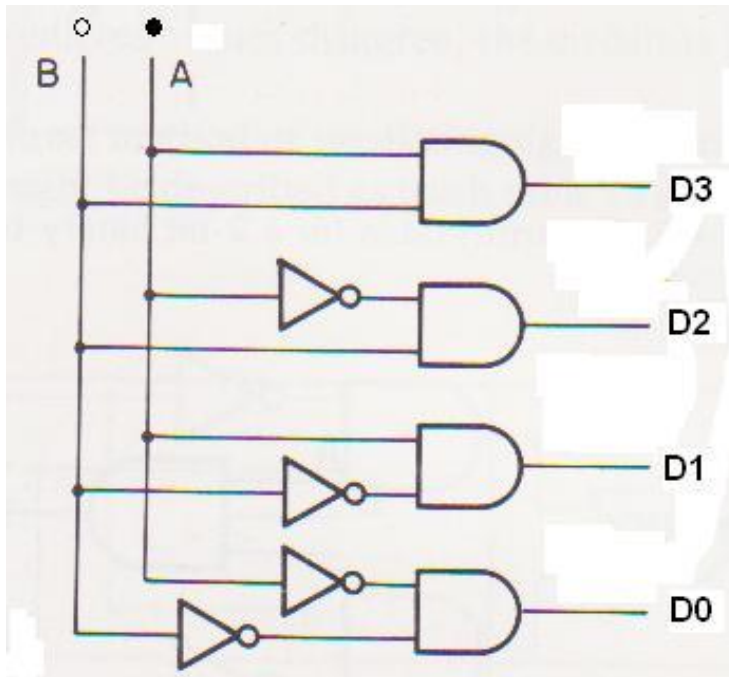9. Record the output for D0, D1, D2, and D3. What decimal value is represented by these binary digits?



Decimal Value _____ (5 points)

D3 = _____ (3 points)

D2 = _____ (3 points)

D1 = _____ (3 points)

D0 = _____ (3 points)

10. Write the Boolean expressions for the logic diagram shown in problem 7. (5 points each)